




ĐẠI HỌC QUỐC GIA THÀNH PHỐ HỒ CHÍ MINH  
**TRƯỜNG ĐẠI HỌC KHOA HỌC TỰ NHIÊN**  
**KHOA ĐIỆN TỬ - VIỄN THÔNG**

# THIẾT KẾ VI MẠCH ĐIỆN TỬ

**EXCERSISES**

**LÊ ĐỨC HÙNG**

 

## EXERCISES

1. Find  $x_p$ ,  $x_n$ ,  $x_d$ ,  $\psi_0$ ,  $C_{j0}$ ,  $C_j$  for an applied voltage of -4V of a pn diode with a step junction,  $N_A = 5 \times 10^{15}/\text{cm}^3$ ,  $N_D = 10^{20}/\text{cm}^3$ , and an area of  $10\mu\text{m}$  by  $10\mu\text{m}$ .
2.  $N_A = 5 \times 10^{15}/\text{cm}^3$ ,  $N_D = 10^{20}/\text{cm}^3$ ,  $D_N = 20\text{cm}^2/\text{s}$ ,  $D_P = 10\text{cm}^2/\text{s}$ ,  $L_N = 10\mu\text{m}$ ,  $L_P = 5\mu\text{m}$ ,  $A = 10\mu\text{m}^2$ . Calculate the saturation current of pn junction.
3. Using LTSPICE, sketch  $I_D$ - $V_{DS}$  characteristic of NMOS and PMOS ( $V_{GS}$  steps from 1V, 2V, 3V, 4V, 5V) for each following transistor sizes:  $W/L = 10\mu\text{m}/10\mu\text{m}$ ,  $W/L = 10\mu\text{m}/1\mu\text{m}$ ,  $W/L = 1\mu\text{m}/10\mu\text{m}$ ,  $W/L = 1\mu\text{m}/1\mu\text{m}$ .
4. Using LTSPICE, sketch  $I_D$ - $V_{GS}$  characteristic of NMOS and PMOS ( $V_{DS}$  steps from 1V, 2V, 3V, 4V, 5V) for each following transistor sizes:  $W/L = 10\mu\text{m}/10\mu\text{m}$ ,  $W/L = 10\mu\text{m}/1\mu\text{m}$ ,  $W/L = 1\mu\text{m}/10\mu\text{m}$ ,  $W/L = 1\mu\text{m}/1\mu\text{m}$ .
5. Using LTSPICE, sketch  $R_{ON}$ - $V_{GS}$  characteristic of NMOS and PMOS with the following transistor sizes:  $W/L = 50\mu\text{m}/1\mu\text{m}$ ,  $W/L = 10\mu\text{m}/1\mu\text{m}$ ,  $W/L = 5\mu\text{m}/1\mu\text{m}$ ,  $W/L = 1\mu\text{m}/1\mu\text{m}$ .

## EXERCISES

6. Consider an NMOS process technology for which  $L_{min} = 0.4\mu m$ ,  $t_{ox} = 8nm$ ,  $m_n = 450cm^2/Vs$ ,  $V_t = 0.7V$ .
- a) Find  $C_{ox}$  and  $k'_n$ .
  - b) For a MOSFET with  $W/L = 8\mu m/0.8\mu m$ , calculate the values of  $v_{OV}$ ,  $v_{GS}$ , and  $v_{DSmin}$  needed to operate the transistor in the saturation region with dc current  $I_D = 100\mu A$ .
  - c) For the device in (b), find the values of  $v_{OV}$  and  $v_{GS}$  required to cause the device to operate as a  $1k\Omega$  resistor for very small  $v_{DS}$ .
7. Consider an NMOS transistor fabricated in an  $0.18\mu m$  process with  $L = 0.18\mu m$  and  $W = 2\mu m$ . The process technology is specified to have  $C_{ox} = 8.6fF/\mu m^2$ ,  $m_n = 450cm^2/Vs$ , and  $V_{tn} = 0.5V$ .
- a) Find  $V_{GS}$  and  $V_{DS}$  that result in the MOSFET operating at the edge of saturation with  $I_D = 100\mu A$ .
  - b) If  $V_{GS}$  is kept constant, find  $V_{DS}$  that results in  $I_D = 50\mu A$ .
  - c) To investigate the use of the MOSFET as a linear amplifier, let it be operating in saturation with  $V_{DS} = 0.3V$ . Find the change in  $i_D$  resulting from  $v_{GS}$  changing from  $0.7V$  by  $+0.01V$  and  $-0.01V$ .

## EXERCISES

8. An inverter is designed with  $(W/L)_n = 10$  and  $(W/L)_p = 16$ , which is fabricated in a process where  $K'_n = 110\mu A/V^2$ ,  $V_{T0n} = 0.7V$ ,  $K'_p = 50\mu A/V^2$ ,  $V_{T0p} = -0.7V$ .
  - a) Calculate the middle point voltage of the inverter  $V_I$ ,  $V_{IH}$ ,  $V_{IL}$ . Make sure that  $V_{IL} < V_I < V_{IH}$ . Use LTSPICE to sketch  $V_{in}$ - $V_{out}$  function waveform, and Voltage Transfer Characteristic (VTC) curve.
  - b) Adjust  $(W/L)_n$  and  $(W/L)_p$  so that the the middle point voltage is at the center of VTC. Use LTSPICE to sketch  $V_{in}$ - $V_{out}$  function waveform, and Voltage Transfer Characteristic (VTC) curve.
9. Calculate the middle point voltage  $V_I$ , of NAND-2 and NOR-2 with  $(W/L)_n = 5$  and  $(W/L)_p = 8$ , which is fabricated in a process where  $K'_n = 110\mu A/V^2$ ,  $V_{T0n} = 0.7V$ ,  $K'_p = 50\mu A/V^2$ ,  $V_{T0p} = -0.7V$ . Use LTSPICE to sketch Voltage Transfer Characteristic (VTC) curve of NAND2 and NOR2.

## EXERCISES

10. Calculation all of the inverter characteristics with the information provided.

PMOS Parameters	NMOS Parameters
$L = 1\mu\text{m}, W = 7\mu\text{m}$	$L = 1\mu\text{m}, W = 5\mu\text{m}$
$V_{Tn} = 0.7\text{V}, K'_n = 110\mu\text{A/V}^2$	$V_{Tp} = -0.8\text{V}, K'_p = 50\mu\text{A/V}^2$
$C_{j0} = 2.82 \times 10^{-8}\text{F/cm}^2, \phi_o = 0.9\text{V}$	$C_{j0} = 4.85 \times 10^{-8}\text{F/cm}^2, \phi_o = 0.92\text{V}$
$C_{jsw} = 4.62 \times 10^{-12}\text{F/cm}, \phi_{osw} = 0.95\text{V}$	$C_{jsw} = 1.95 \times 10^{-12}\text{F/cm}, \phi_{osw} = 0.97\text{V}$
Oxide thickness: $t_{ox} = 150 \text{ \AA}$	
Gate overlap: $L_o = 0.05\mu\text{m}$	
Power supply: $V_{DD} = 5\text{V}$	
Fanout number: $FO = 3$	

## EXERCISES

11. Calculation of setup time and hold time. Are there any violations of Setup time and Hold time?

